

CS64 Week 5 Lecture I

Kyle Dewey

Overview

- Recursion in the MIPS calling convention
- Tail call optimization
- Introduction to circuits
- Digital design: single bit adders
- Karnaugh maps

Recursion in MIPS

Quick MIPS Calling Convention Review

- `nested_calls.asm`
- `save_registers.asm`

Recursion

- This same setup handles nested function calls and recursion - we can save `$ra` on the stack
- **Example:** `recursive_fibonacci.asm`

More Recursion

- What's special about the following recursive function?

```
int recFac(int n, int accum) {  
    if (n == 0) {  
        return accum;  
    } else {  
        return recFac(n - 1, n * accum);  
    }  
}
```

More Recursion

- What's special about the following recursive function?
 - It is *tail recursive* - with the right optimization, uses constant stack space
 - We can do this in assembly -
`tail_recursive_factorial.asm`

```
int recFac(int n, int accum) {  
    if (n == 0) {  
        return accum;  
    } else {  
        return recFac(n - 1, n * accum);  
    }  
}
```

Dispelling the Magic: Circuits

Why Binary?

- Very convenient for a circuit
 - Two possible states: on and off
 - 0 and 1 correspond to on and off

Relationship to Bitwise Operations

- You're already familiar with bitwise OR, AND, XOR, and NOT
- These same operations are fundamental to circuits
 - Basic building blocks for more complex things

Single Bits

- For the moment, we will deal only with individual bits
- Later, we'll see this isn't actually that restrictive

Operations on Single Bits: AND





Operations on Single Bits: OR




Operations on Single Bits: XOR



Operations on Single Bits: NOT

  


Recall: Single Bit Adders

 


–We had defined a single bit adder that worked like the above...


Stringing them Together

 For two three-bit numbers, A and B , resulting in
a three-bit result R



 

As a Truth Table

 


C_I	I_1	I_2	C_O	R
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

–Inputs and outputs are separated by a line

As a Truth Table

 Question: how can this be turned into a circuit?



C_I	I_1	I_2	C_O	R
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

–As in, how can we utilize the gates from before to implement this?

Sum of Products

- Variables: $A, B, C...$
- Negation of a variable: $\overline{A}, \overline{B}, \overline{C}...$

–Negating a variable is denoted by putting a bar above it

Sum of Products

- Another way to look at OR: sum (+)

$$A + B$$

- Another way to look at AND: multiplication (*)

$$A * B$$

$$AB$$

Sum of Products

Example

A	B	O
0	0	0
0	1	1
1	0	1
1	1	0

–Say we have this truth table

Sum of Products Example

A	B	O
0	0	0
0	1	1
1	0	1
1	1	0

–We look at the rows with a 1 result

Sum of Products

Example

A	B	O
0	0	0
0	1	1
1	0	1
1	1	0

$$O = \overline{A} * B$$

–For each such row, we generate a product

Sum of Products

Example

A	B	O
0	0	0
0	1	1
1	0	1
1	1	0

$$O = \overline{A} * B + A * \overline{B}$$

–For each such row, we generate a product

Sum of Products

C_I	I_1	I_2	C_O	R
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Question: What would the sum of products look like for this table?
(Note: need one equation for each output.)

Sum of Products

C_I	I_1	I_2	C_O	R
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Question: What would the sum of products look like for this table?
(Note: need one equation for each output.)

Answer in the presenter notes.

-Using $\neg A$ to mean the negation of A
 $C_O = \neg C_I \cdot I_1 \cdot I_2 + C_I \cdot \neg I_1 \cdot I_2 + C_I \cdot I_1 \cdot \neg I_2 + C_I \cdot I_1 \cdot I_2$
 $R = \neg C_I \cdot \neg I_1 \cdot I_2 + \neg C_I \cdot I_1 \cdot \neg I_2 + C_I \cdot \neg I_1 \cdot \neg I_2 + C_I \cdot I_1 \cdot I_2$

In-Class Example: Shift Left by 1

Karnaugh Maps

Motivation

- Unnecessarily large programs: bad
- Unnecessarily large circuits: Very Bad™
 - Why?

Motivation

- Unnecessarily large programs: bad
- Unnecessarily large circuits: Very Bad™
 - Why?
 - Bigger circuits = bigger chips = higher cost (non-linear too!)
 - Longer circuits = more time needed to move electrons through = slower

Simplification

- Real-world formulas can often be simplified
 - How might we simplify the following?

$$R = A * B + !A * B$$

–How might we simplify this?

Simplification

- Real-world formulas can often be simplified
 - How might we simplify the following?

$$R = A * B + !A * B$$

$$R = B (A + !A)$$

$$R = B (\text{true})$$

$$R = B$$

Scaling Up

- Performing this sort of algebraic manipulation by hand can be tricky
- We can use *Karnaugh maps* to make it immediately apparent as to what can be simplified

Example

$$R = A * B + !A * B$$

–Start with the sum of products

Example

$$R = A * B + !A * B$$

A	B	O
0	0	0
0	1	1
1	0	0
1	1	1

–Build the truth table

Example

$$R = A * B + !A * B$$

A	B	O
0	0	0
0	1	1
1	0	0
1	1	1


		B	
A		0	1
0		0	1
1		0	1

–Build the K-map

Example

$$R = A * B + !A * B$$

A	B	O
0	0	0
0	1	1
1	0	0
1	1	1

 


-Group adjacent (row or column-wise, NOT diagonal) 1's in powers of two (groups of 2, 4, 8...)

-

Example

$$R = A * B + !A * B$$

A	B	O
0	0	0
0	1	1
1	0	0
1	1	1

 


- The values that stay the same are saved, the rest are discarded
- This works because this means that the inputs that differ are irrelevant to the final value, and so they can be removed

Example

$$R = A * B + !A * B$$

A	B	O
0	0	0
0	1	1
1	0	0
1	1	1

 

- The values that stay the same are saved, the rest are discarded
- This works because this means that the inputs that differ are irrelevant to the final value, and so they can be removed

Three Variables

- We can scale this up to three variables, by combining two variables on one axis
- The combined axis must be arranged such that only one bit changes per position

		BC			
		00	01	11	10
A	0	?	?	?	?
	1	?	?	?	?

Three Variable Example

$$R = !A!BC + !ABC + A!BC + ABC$$

–Start with this formula

$$R = !A!BC + !ABC + A!BC + ABC$$

A	B	C	R
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

–Build the truth table

$$R = !A!BC + !ABC + A!BC + ABC$$


A	B	C	R
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

		BC			
A		00	01	11	10
0		0	1	1	0
1		0	1	1	0

–Build the K-map

$$R = !A!BC + !ABC + A!BC + ABC$$

A	B	C	R
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

 


- Select the biggest group possible, in this case a square
- In order to get the most minimal circuit, we must always select the biggest groups possible

$$R = !A!BC + !ABC + A!BC + ABC$$

A	B	C	R
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

$$R = C$$

 

-Save the ones that stay the same in a group, discarding the rest

Another Three Variable Example

$$R = !A!B!C + !A!BC + !ABC + \\ !AB!C + A!B!C + AB!C$$

–Start with this formula

$$R = !A!B!C + !A!BC + !ABC + !AB!C + A!B!C + AB!C$$

A	B	C	R
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

–Build the truth table

$$R = !A!B!C + !A!BC + !ABC + !AB!C + A!B!C + AB!C$$

A	B	C	R
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

		BC			
A		00	01	11	10
0		1	1	1	1
1		1	0	0	1

–Build the K-map

$$R = !A!B!C + !A!BC + !ABC + !AB!C + A!B!C + AB!C$$


A	B	C	R
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

		BC			
A		00	01	11	10
0		1	1	1	1
1		1	0	0	1

- Select the biggest groups possible
- Note that the values “wrap around” the table

$$R = !A!B!C + !A!BC + !ABC + !AB!C + A!B!C + AB!C$$


A	B	C	R
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

 

- Save the ones that stay the same in a group, discarding the rest
- This must be done for each group

$$R = !A!B!C + !A!BC + !ABC + !AB!C + A!B!C + AB!C$$

A	B	C	R
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

 


- Save the ones that stay the same in a group, discarding the rest
- This must be done for each group

$$R = !A!B!C + !A!BC + !ABC + !AB!C + A!B!C + AB!C$$

A	B	C	R
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

$$R = !A + !C$$

 

- Save the ones that stay the same in a group, discarding the rest
- This must be done for each group

Four Variable Example

$$R = !A!B!C!D + !A!B!CD + !A!BC!D + \\ !ABC!D + A!B!C!D + A!B!CD + A!BC!D$$


–Take this formula

$$R = !A!B!C!D + !A!B!CD + !A!BC!D + !ABC!D + A!B!C!D + A!B!CD + A!BC!D$$

		CD			
		00	01	11	10
AB	00	1	1	0	1
	01	0	0	0	1
	11	0	0	0	0
	10	1	1	0	1

–For space reasons, we go directly to the K-map
 
$$R = !A!B!C!D + !A!B!CD + !A!BC!D + !ABC!D + A!B!C!D + A!B!CD + A!BC!D$$



- Group things up
- The edges logically wrap around!
- Groups may overlap each other

$$R = !A!B!C!D + !A!B!CD + !A!BC!D + !ABC!D + A!B!C!D + A!B!CD + A!BC!D$$

$$R = !B!C$$

		CD			
		00	01	11	10
AB	00	1	1	0	1
	01	0	0	0	1
	11	0	0	0	0
	10	1	1	0	1

- Look at the bits that don't change
- First for the cube

$$R = !A!B!C!D + !A!B!CD + !A!BC!D + !ABC!D + A!B!C!D + A!B!CD + A!BC!D$$

$$R = !B!C + !B!D$$

		CD			
AB		00	01	11	10
	00	1	1	0	1
	01	0	0	0	1
	11	0	0	0	0
	10	1	1	0	1

- Look at the bits that don't change
- Second for the cube on the edges

$$R = !A!B!C!D + !A!B!CD + !A!BC!D + !ABC!D + A!B!C!D + A!B!CD + A!BC!D$$

$$R = !B!C + !B!D + !AC!D$$

		CD			
AB		00	01	11	10
00		1	1	0	1
01		0	0	0	1
11		0	0	0	0
10		1	1	0	1

- Look at the bits that don't change
- Third for the line

K-Map Rules in Summary (I)

- Groups can contain only 1s
- Only 1s in adjacent groups are allowed (no diagonals)
- The number of 1s in a group must be a power of two (1, 2, 4, 8...)
- The groups must be as large as legally possible

K-Map Rules in Summary (2)

- All 1s must belong to a group, even if it's a group of one element
- Overlapping groups are permitted
- Wrapping around the map is permitted
- Use the fewest number of groups possible